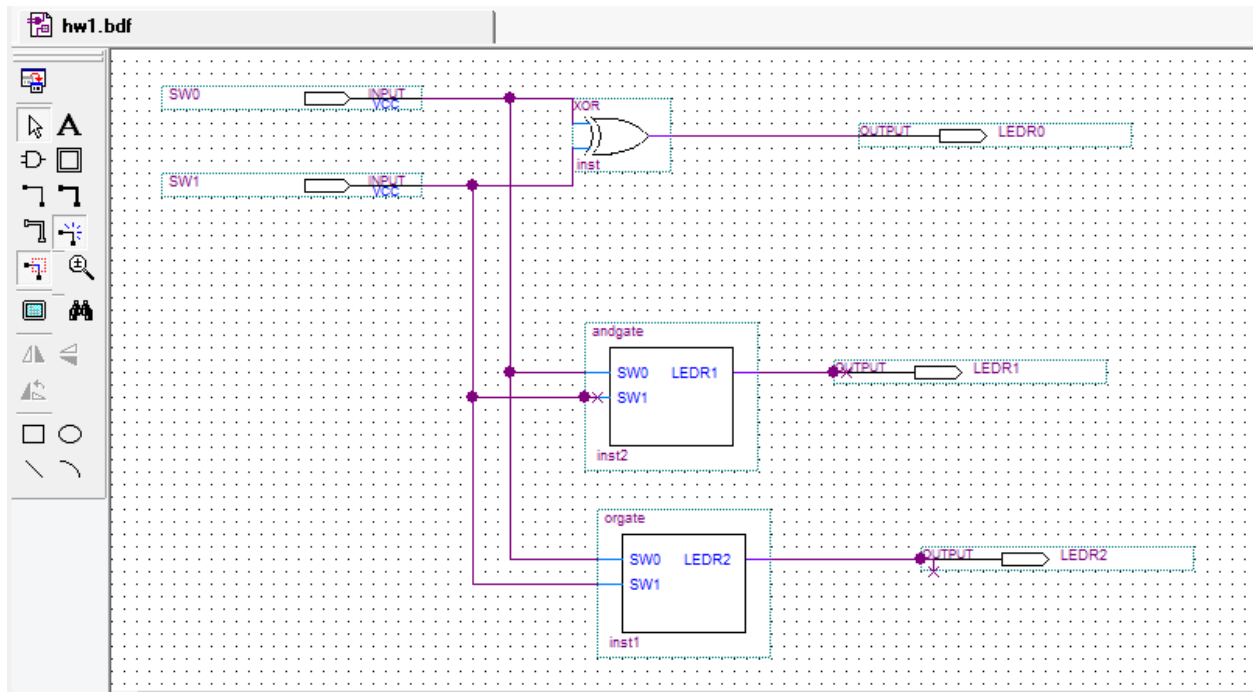


## BDF Top Level



## Verilog Source (orgate.v)

```
module orgate
(
    input SW0, SW1,
    output LEDR2
);

assign LEDR2 = SW0 | SW1;

endmodule
```

## VHDL Source (andgate.vhd)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity andgate is

    port
    (
        SW0, SW1      : in std_logic;
        LEDR1         : out std_logic

    );

end entity;

architecture rtl of andgate is
begin

    LEDR1 <= SW0 AND SW1;
end rtl;
```

## Simulation

